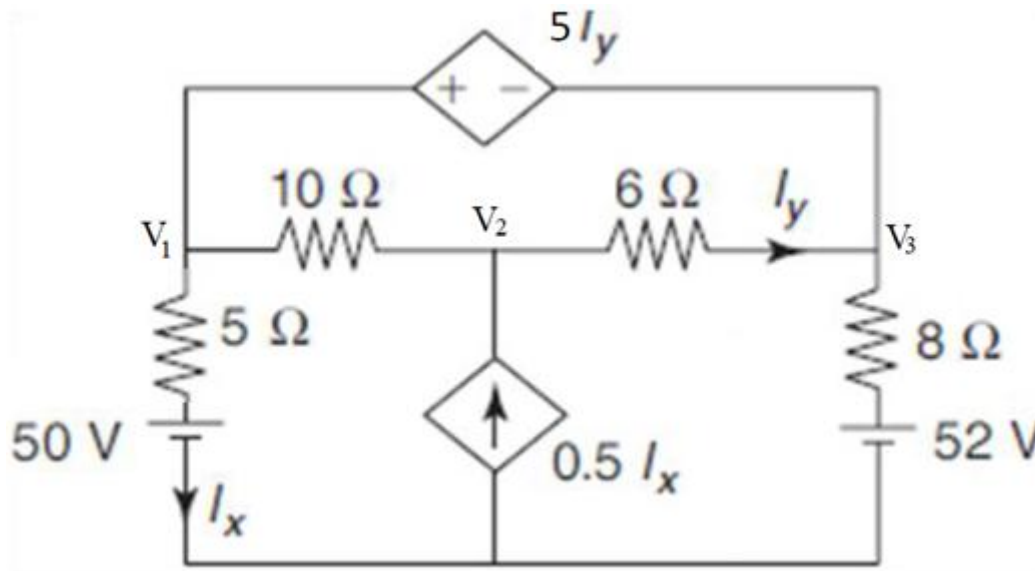



Nodal analysis of DC circuits and AC circuits

Assignment / hands-on Slot 1

1. Determine the unknown nodal voltages in the circuit given below. Draw and simulate the given circuit in QUCS and verify your calculation. Submit your calculation and screenshot of the circuit and results observed in QUCS.



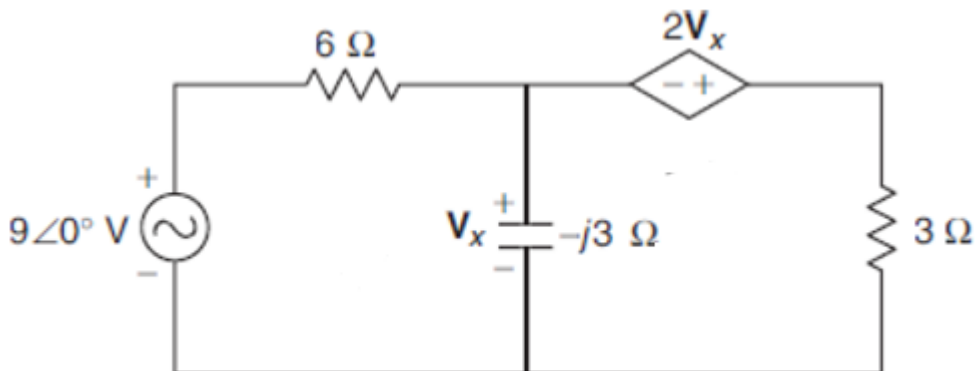2. Find the nodal voltage V_x in the circuit given below. Verify your results using simulation in QUCS. Submit your calculation and screenshot of the circuit and results observed in QUCS.



Submission should be done via online (link will be provided for uploading the answers).

Deadline for submission: Next day after your A/H/P slot