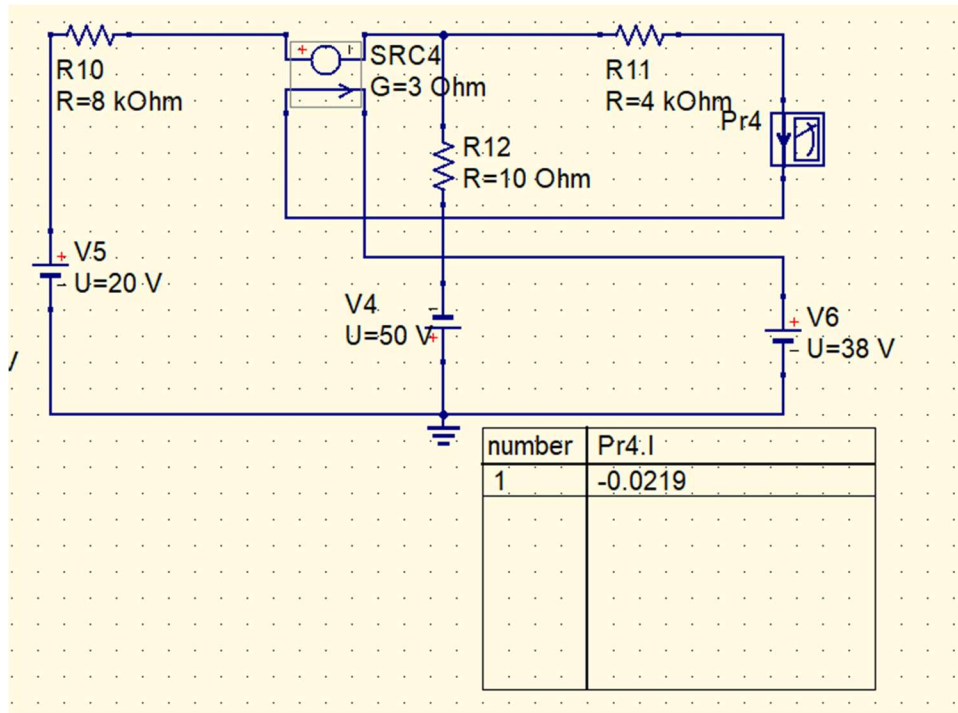



SUPERPOSITION THEOREM – A/H/P 2

PROBLEM 1- DC


a) All sources considered




b) 20V source

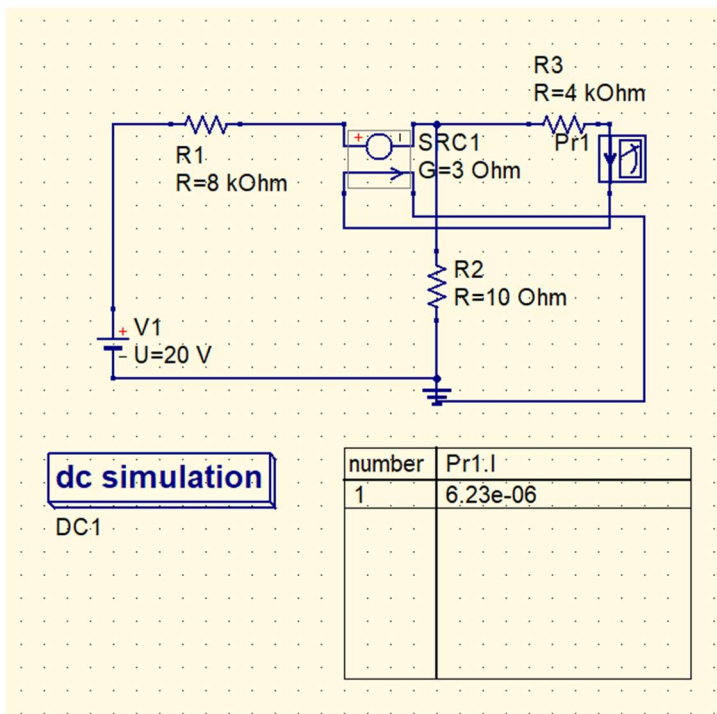

c) 50V source

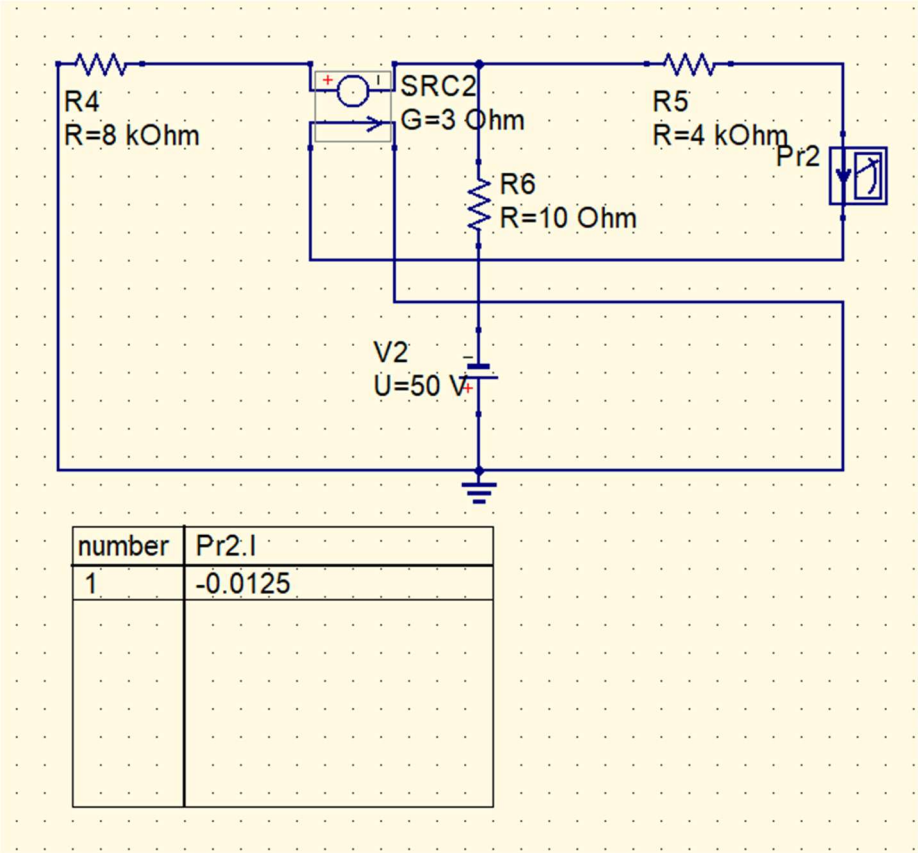


d) 38V source

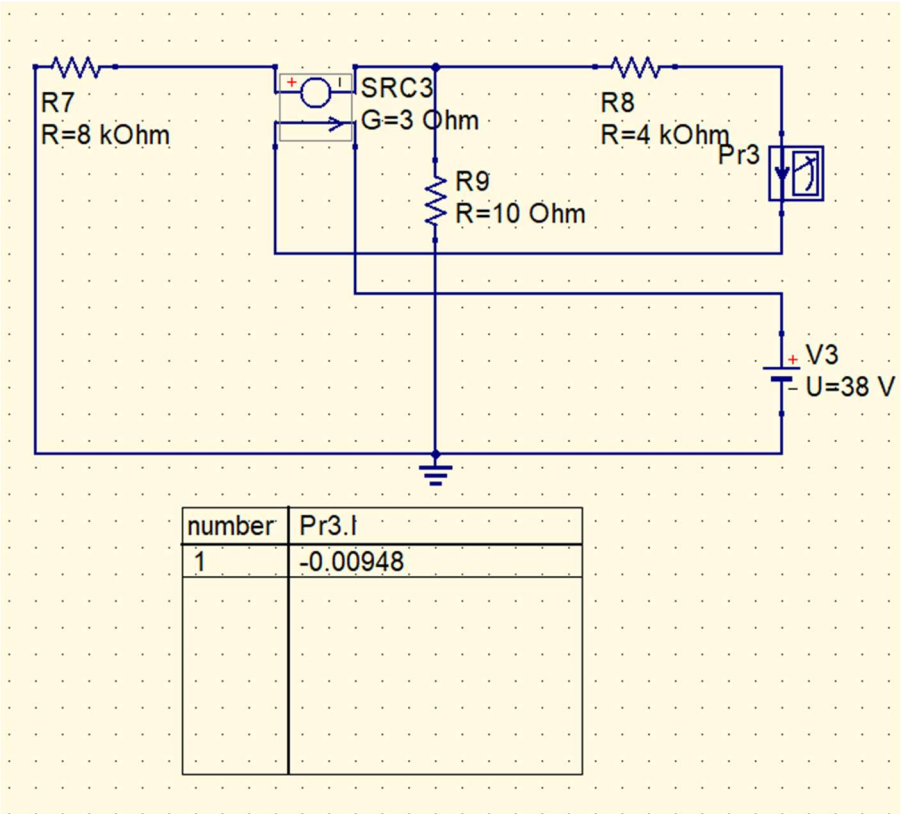


2. PROBLEM 2- AC

a) All sources considered

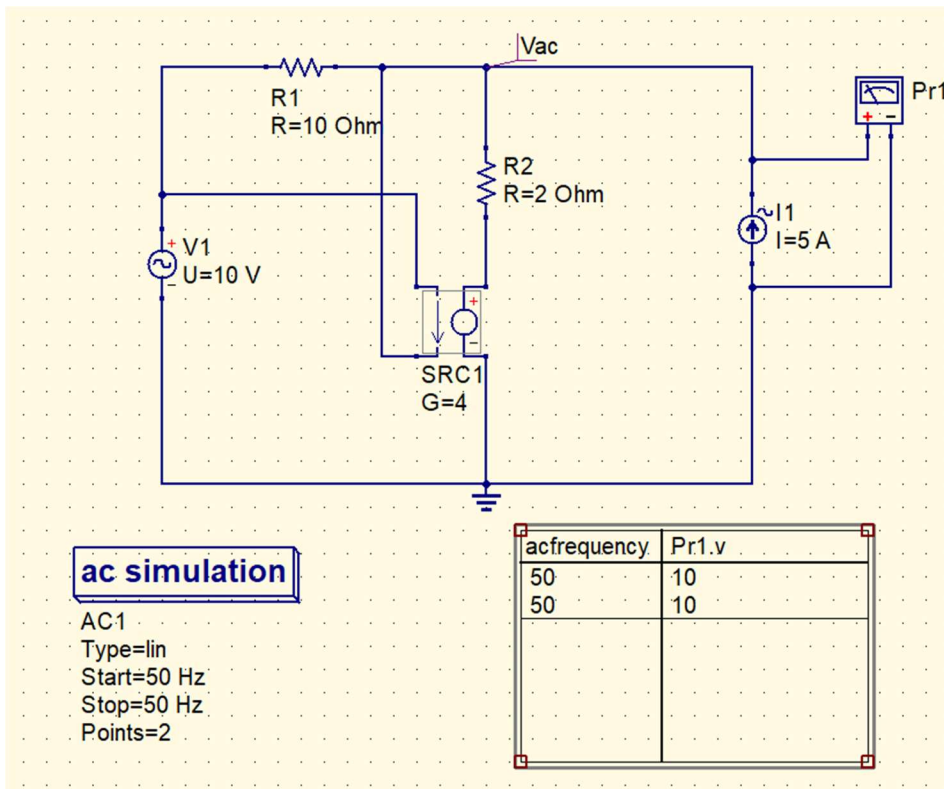

b) 10V source

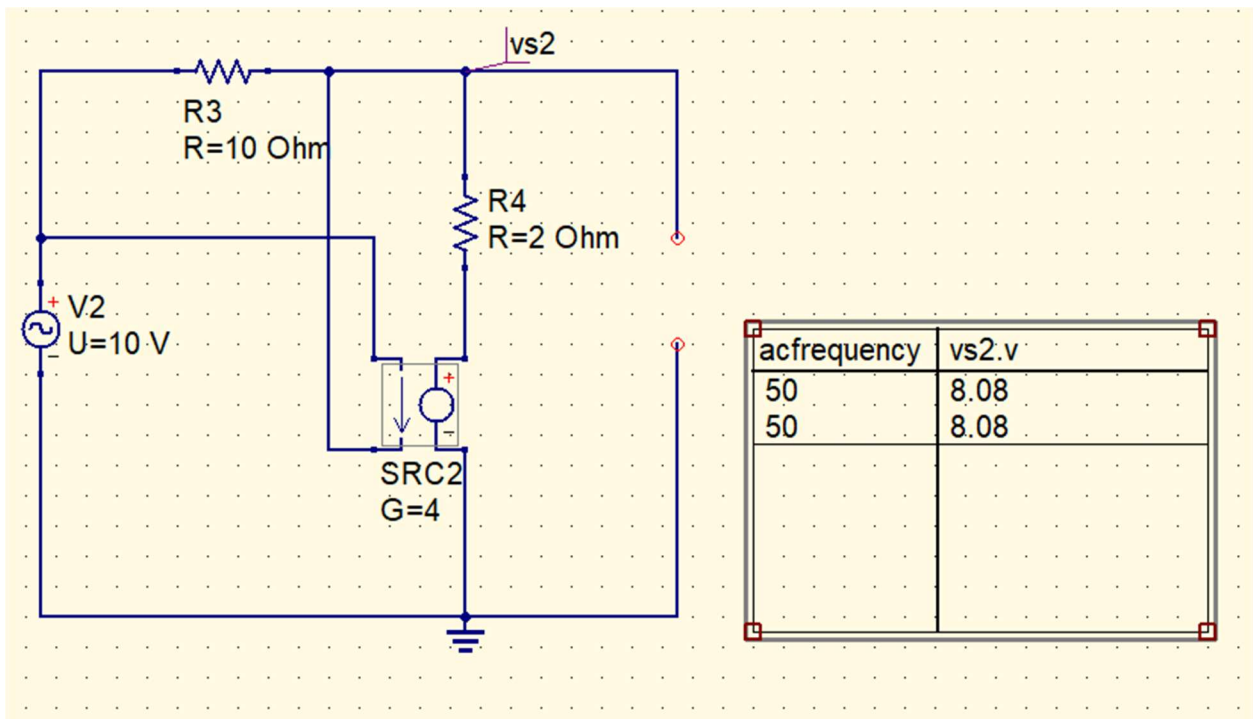

c) 5A source

